


160 Meter

Mickey Mouse

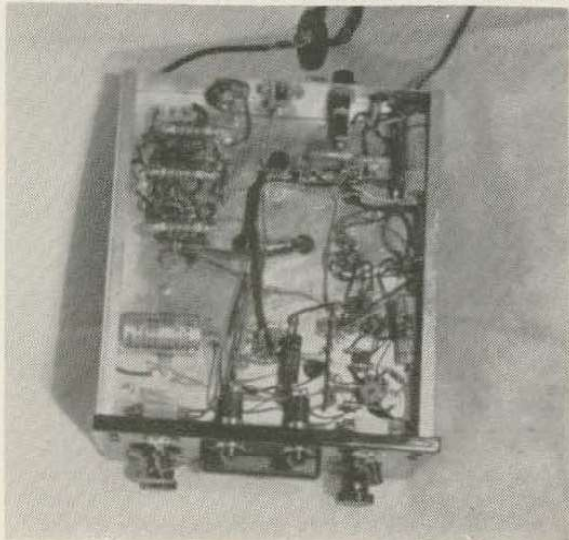C. L. Martin K9PAL
Instrument & Electronic Tech.
General Electric Company
Bloomington, Illinois

WITH the increased amount of activity on the amateur bands these days, it becomes even more difficult to find the frequency space to carry on the famous "rag chew" session with the local brothers of the profession without "tromping" on some poor soul in the next state who is trying to stretch some range out of the "Half Quart" rig, or move that piece of traffic thru the QRM. Faced with these problems, it becomes even more sensible to make use of that 25 kilocycle hunk of frequency in the 160 meter band for the "local" activity. Range of 25 miles or so is consistent on these frequencies with occasional real DX reported on quite low power. So, to this I add the question "Why not a rig that is portable enough to carry to the over night fishing hole or on the vacation"? The rig described here, combined with a "tuned over" AC/DC set or, small portable provides this portability as well as reasonable power on a vertical or half of the old 75 meter dipole.

Circuit and construction is along conventional lines with the exception of the power supply, which is less common. Here the circuit makes use of a pair of the modern silicon rectifiers in a half wave doubler circuit run-



ning straight out of the 115 volt line. Two things are accomplished by this. First the familiar power transformer is absent (a sizeable cost reduction) and second, the ac ground system is used to advantage with the portable whip. To do this without making the cabinet "hot," a built in line polarity indicator is used. With the power switch OFF and the chassis connected to the line "hot" side, the neon will provide enough glow thru leakage to be seen, even if no ground is present on the cabinet. If the neon glows, the line plug need only be turned $\frac{1}{2}$ turn to correctly polarize. A 2 amp fuse in the ground side provides protection in case of a mistake in polarity when the rig is attached to an earth ground. Such a system is not dangerous when handled properly. It is strongly advised that an earth ground be attached to the cabinet whenever possible, however.

Parts placement is not critical and no shielding between components should be necessary. It is suggested that the modulator be placed as far as possible on the chassis from the rf section. The familiar 6L6 was selected for the final stage because it operates efficiently at the relatively low plate voltage and is usually readily available from the junk box. Grid drive should be adequate when the OSC tuning coil is peaked. If more drive is required, this can be accomplished by decreasing the 20K dropping resistor in the oscillator plate. Grid drive should be near 3 ma.

Although the final is capable of more than the 18 watts indicated, the modulator is good for only about 9 watts. If 100% modulation is to be realized the final must be held down to this value.

